

Computer Organization and Architecture		
Lab #:	11	
Lab Title:	Combinational and Sequential circuits	
Submitted by:		
Names		Registration #
Sumaira Safeer		FA22-BCE-019

Rubrics name & number					Marks	
					In-Lab	Post-Lab
Engineering Knowledge	R2: Use of Engineering Knowledge and follow Experiment Procedures: <i>Ability to follow experimental procedures, control variables, and record procedural steps on lab report.</i>					
Problem Analysis	R6: Experimental Data Analysis: <i>Ability to interpret findings, compare them to values in the literature, identify weaknesses and limitations.</i>					
Design	R8: Best Coding Standards: <i>Ability to follow the coding standards and programming practices.</i>					
Modern Tools Usage	R9: Understand Tools: <i>Ability to describe and explain the principles behind and applicability of engineering tools.</i>					
Individual and Teamwork	R12: Individual Work Contributions: <i>Ability to carry out individual responsibilities.</i>					
	R13: Management of Team Work: <i>Ability to appreciate, understand and work with multidisciplinary team members.</i>					
Rubrics #	R2	R6	R8	R9	R12	R13
In Lab						
Post- Lab						

Combinational and Sequential circuits


Objectives:

This lab includes a refresher of combinational and sequential circuits.

- Review/refresher of combinational circuits.
- Review/refresher of sequential circuits.

Task 1:

Five-input and-or-invert (AOI) circuit.

 

Verilog Code:

```
module AOI5_CA0 (y_out, x_in);
input [4:0] x_in; // Inputs of UUT decided as ?reg?
output y_out; //Outputs of UUT (is this case module verilog?)

assign y_out = ~((x_in[0] & x_in[1])|(x_in[2]& x_in[3]& x_in[4]));
endmodule
```

TestBench:


```
module TB_AOI5_CA0;
reg [4:0] x_in; // Inputs of UUT decided as ?reg?
wire y_out; //Outputs of UUT (is this case module verilog?) decided as // wire
```

```

AOI5_CA0 uut (           // Instantiate the Unit Under Test (UUT)
    .x_in(x_in),
    .y_out(y_out)
);
initial begin
    // Apply test cases
    x_in = 5'b00000;
    #10;           // All inputs 0
    x_in = 5'b00011;
    #10;           // x_in[0]=1, x_in[1]=1
    x_in = 5'b11100;
    #10;           // x_in[2]=1, x_in[3]=1, x_in[4]=1
    x_in = 5'b11111;
    #10;           // All inputs 1
    x_in = 5'b10101;
    #10;           // Mixed inputs
    x_in = 5'b01010;
    #10;           // Alternate inputs
    $stop;         // End simulation
end
endmodule

```

Result:

 

Task 2:

implements a 32-bit 4-1 mux using conditional operator.

Verilog Code:

```
module mux_4_to_1 (
    input [31:0] I0, // 32-bit input 0
    input [31:0] I1, // 32-bit input 1
    input [31:0] I2, // 32-bit input 2
    input [31:0] I3, // 32-bit input 3
    input S1,      // Select line 1
    input S0,      // Select line 0
    output reg [31:0] Y // 32-bit output
);
always @(*) begin
    // Case structure to implement the 4-to-1 MUX
    case ({S1, S0})
        2'b00: Y = I0; // When S1=0, S0=0, output I0
        2'b01: Y = I1; // When S1=0, S0=1, output I1
        2'b10: Y = I2; // When S1=1, S0=0, output I2
    endcase
end
```

```

2'b11: Y = I3; // When S1=1, S0=1, output I3

    default: Y = 32'b0; // Default case (safe, if needed)

endcase

end

endmodule

```

TestBench:

```

module tb_mux_4_to_1;

    // Declare inputs as reg and output as wire
    reg [31:0] I0, I1, I2, I3;    // Inputs of UUT decided as ?reg?
    reg S1, S0;
    wire [31:0] Y;                //Outputs of UUT (is this case module verilog?) //wire

    mux_4_to_1 uut (              // Instantiate the MUX module
        .I0(I0),
        .I1(I1),
        .I2(I2),
        .I3(I3),
        .S1(S1),
        .S0(S0),
        .Y(Y)
    );

    initial begin
        // Initialize inputs
        I0 = 32'h12345678;
        I1 = 32'h23456789;
        I2 = 32'h34567890;
        I3 = 32'h45678901;

        S1 = 0; S0 = 0;           // Instantiate the MUX module    // Select I0
    end

```

```

#10;

$display("S1=%b S0=%b, Y=%h", S1, S0, Y);

S1 = 0; S0 = 1;          // Select I1

#10;

$display("S1=%b S0=%b, Y=%h", S1, S0, Y);


S1 = 1; S0 = 0;          // Select I2

#10;

$display("S1=%b S0=%b, Y=%h", S1, S0, Y);


S1 = 1; S0 = 1;          // Select I3

#10;

$display("S1=%b S0=%b, Y=%h", S1, S0, Y);

$finish;

end

endmodule

```

Result:

